



Module 2 – Part 5

Introduction to Verilog



Hardware Description Languages

- We have studied two languages:
 - System Verilog
 - VHDL
- Verilog is older than VHDL:
 - Similar to Pascal and C
 - Delays is the only interaction with Simulator
 - Fairly Efficient and easy to write
 - IEEE Standard
- Li MIPS Architecture is written in Verilog




Tutorial Plan




- Structural Models
- Combinational Behavior Models
- Syntax
- Examples
- Testbench

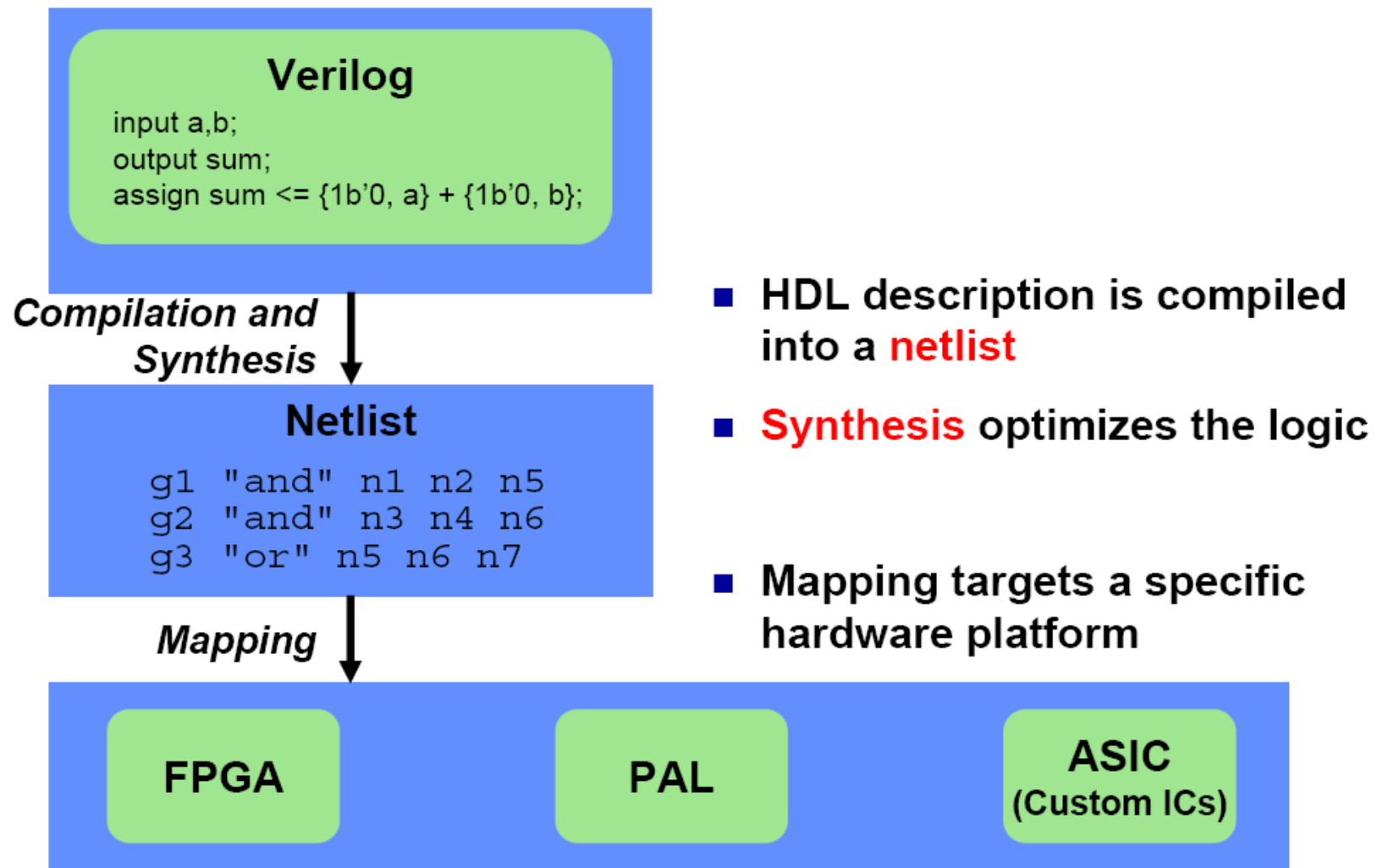- Hardware description language (HDL) is a convenient, device-independent representation of digital logic



Design Methodology

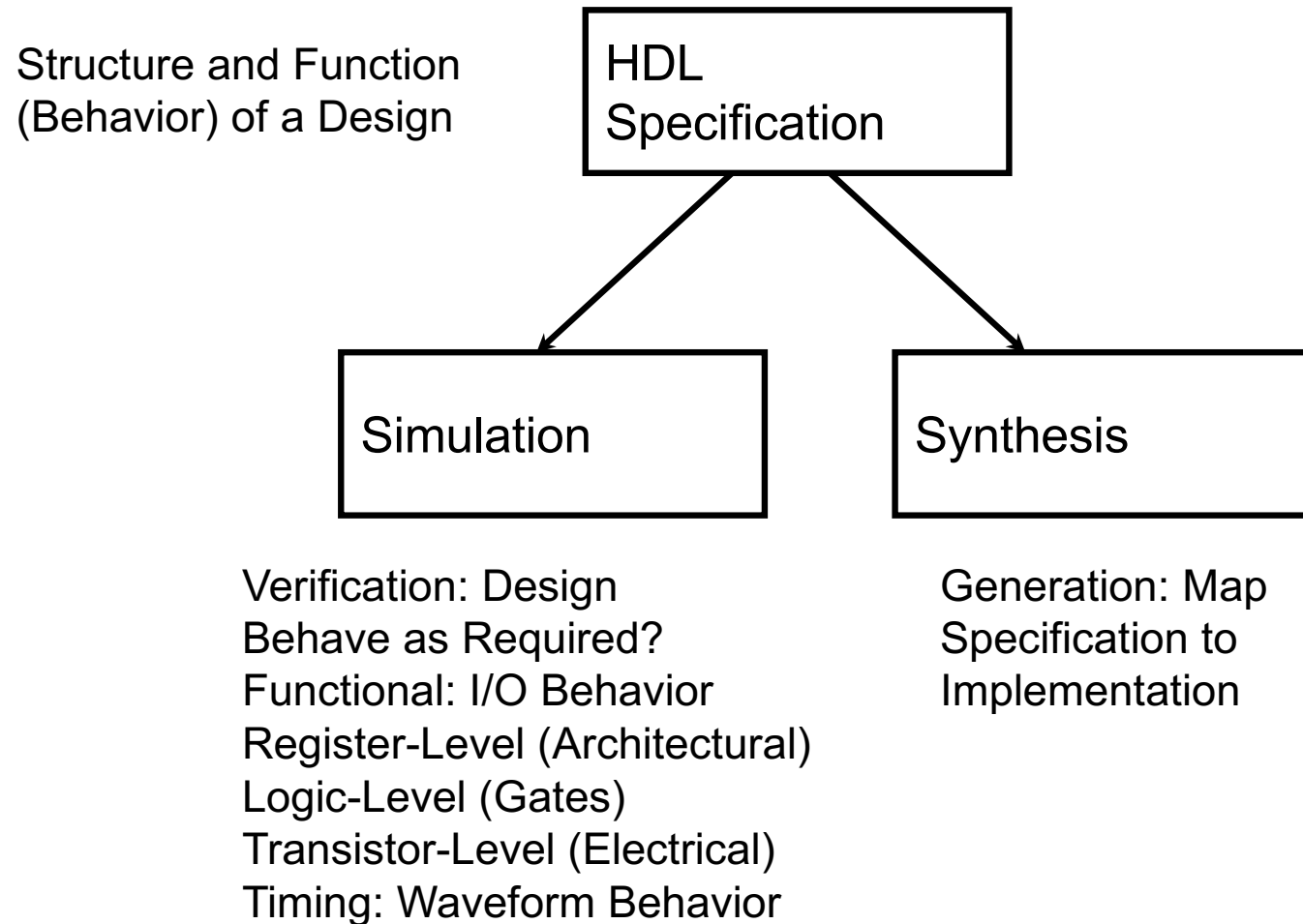



Verilog

- Supports structural and behavioral descriptions
- Structural
 - Explicit structure of the circuit
 - How a module is composed as an interconnection of more primitive modules/components
 - E.g., each logic gate instantiated and connected to others
- Behavioral
 - Program describes input/output behavior of circuit
 - Many structural implementations could have same behavior
 - E.g., different implementations of one Boolean function



Verilog Introduction

- the module describes a component in the circuit
- Two ways to describe:
 - Structural Verilog
 - List of components and how they are connected
 - Just like schematics, but using text
 - Hard to write, hard to decode
 - Useful if you don't have integrated design tools
 - Behavioral Verilog
 - Describe *what* a component does, not *how* it does it
 - Synthesized into a circuit that has this behavior



Structural Model

- Composition of primitive gates to form more complex module
- Note use of wire declaration!

```
module xor_gate (out, a, b);  
    input      a, b;  
    output     out;  
    wire       abar, bbar, t1, t2;
```

By default, identifiers
are wires

```
    inverter invA (abar, a);  
    inverter invB (bbar, b);  
    and_gate and1 (t1, a, bbar);  
    and_gate and2 (t2, b, abar);  
    or_gate  or1 (out, t1, t2);
```

```
endmodule
```




Structural Model

- Example of full-adder

```
module full_addr (A, B, Cin, S, Cout);  
    input      A, B, Cin;  
    output     S, Cout;
```

```
    assign {Cout, S} = A + B + Cin;  
endmodule
```

Behavior

```
module adder4 (A, B, Cin, S, Cout);  
    input  [3:0] A, B;  
    input          Cin;  
    output [3:0] S;  
    output          Cout;  
    wire         C1, C2, C3;
```

Structural

```
    full_addr fa0 (A[0], B[0], Cin, S[0], C1);  
    full_addr fa1 (A[1], B[1], C1, S[1], C2);  
    full_addr fa2 (A[2], B[2], C2, S[2], C3);  
    full_addr fa3 (A[3], B[3], C3, S[3], Cout);  
endmodule
```



Simple Behavioral Model

- Combinational logic
 - Describe output as a function of inputs
 - Note use of `assign` keyword: *continuous* assignment

```
module and_gate (out, in1, in2);  
    input        in1, in2;  
    output       out;  
  
    assign out = in1 & in2;  
  
endmodule
```

Output port of a *primitive* must be first in the list of ports

Restriction does not apply to *modules*



Verilog Data Types and Values

- Bits - value on a wire
 - 0, 1
 - **x** - don't care/don't know
 - **z** - undriven, tri-state
- Vectors of bits
 - **A[3:0]** - **vector of 4 bits: A[3], A[2], A[1], A[0]**
 - Treated as an *unsigned* integer value
 - e.g., **A < 0** ??
 - Concatenating bits/vectors into a vector
 - e.g., sign extend
 - **B[7:0] = {A[3], A[3], A[3], A[3], A[3:0]};**
 - **B[7:0] = {4{A[3]}, A[3:0]};**
 - Style: Use **a[7:0] = b[7:0] + c;**
Not: **a = b + c;** // need to look at declaration



Verilog Numbers

- **14** - ordinary decimal number
- **-14** - 2's complement representation
- **12'b0000_0100_0110** - binary number with 12 bits
(**_** is ignored)
- **12'h046** - hexadecimal number with 12 bits
- Verilog values are *unsigned*
 - e.g., **C[4:0] = A[3:0] + B[3:0];**
 - if A = 0110 (6) and B = 1010(-6)
C = 10000 not 00000
i.e., B is zero-padded, not sign-extended




Four-valued Data

- Verilog's nets and registers hold four-valued data
- 0, 1
 - Obvious
- Z
 - Output of an undriven tri-state driver
 - Models case where nothing is setting a wire's value
- X
 - Models when the simulator can't decide the value
 - Initial state of registers
 - When a wire is being driven to 0 and 1 simultaneously
 - Output of a gate with Z inputs



Four-valued Logic

 - Logical operators work on three-valued logic



	0	1	X	Z
0	0	0	0	0
1	0	1	X	X
X	0	X	X	X
Z	0	X	X	X

← Output 0 if one input is 0

← Output X if both inputs are gibberish

Verilog Operators

Verilog Operator	Name	Functional Group
()	bit-select or part-select	
()	parenthesis	
! ~ & ~& ~ ^ ~^ or ^~	logical negation negation reduction AND reduction OR reduction NAND reduction NOR reduction XOR reduction XNOR	Logical Bit-wise Reduction Reduction Reduction Reduction Reduction Reduction
+ -	unary (sign) plus unary (sign) minus	Arithmetic Arithmetic
{}	concatenation	Concatenation
{{}}	replication	Replication
* / %	multiply divide modulus	Arithmetic Arithmetic Arithmetic
+ -	binary plus binary minus	Arithmetic Arithmetic
<< >>	shift left shift right	Shift Shift

> >= < <=	greater than greater than or equal to less than less than or equal to	Relational Relational Relational Relational
== !=	logical equality logical inequality	Equality Equality
=== !==	case equality case inequality	Equality Equality
&	bit-wise AND	Bit-wise
^ ^~ or ~^	bit-wise XOR bit-wise XNOR	Bit-wise Bit-wise
	bit-wise OR	Bit-wise
&&	logical AND	Logical
	logical OR	Logical
?:	conditional	Conditional



Verilog “Variables”

- wire
 - Variable used simply to connect components together
- reg
 - Variable that saves a value as part of a behavioral description
 - Usually corresponds to a wire in the circuit
 - Is *NOT* necessarily a register in the circuit
- The Rule:
 - Declare a variable as a `reg` if it is the target of a *concurrent (non-blocking)* assignment statement
 - Don't confuse reg assignments with the combinational continuous `assign` statement!
 - Reg should only be used with `always` blocks (sequential logic, to be presented ...)
 - Confusing isn't it?



Wire Elements

- Wire elements are used to connect input and output ports of a module instantiation together with some other element in your design.
- Wire elements are used as inputs and outputs within an actual module declaration.
- Wire elements must be driven by something, and cannot store a value without being driven.
- Wire elements cannot be used as the left-hand side of an = or <= sign in an always@ block.
- Wire elements are the only legal type on the left-hand side of an Assign statement.
- Wire elements are a stateless way of connecting two pieces in a Verilog-based design.
- Wire elements can only be used to model combinational logic



Register Elements

- Reg Elements can be connected to the input port of a module instantiation.
- Reg Elements cannot be connected to the output port of a module instantiation.
- Reg Elements can be used as Outputs within an actual module declaration.
- Reg Elements cannot be used as inputs within an actual module declaration.
- Reg is the only legal type on the left-hand side of an `always@ Block = Or <= sign`.
- Reg is the only legal type on the left-hand side of an Initial Block = sign (used in Test Benches).
- Reg cannot be used on the left-hand side of an Assign statement.
- Reg can be used to create registers when used in conjunction with `always@(Posedge Clock)` blocks.
- Reg can, therefore, be used to create both combinational and sequential logic.

Verilog Module

- Corresponds to a circuit component
 - “Parameter list” is the list of external connections, aka “ports”
 - Ports are declared “input”, “output” or “inout”
 - inout ports used on tri-state buses
 - Port declarations imply that the variables are wires

module name

ports

```
module full_addr (A, B, Cin, S, Cout);  
  input      A, B, Cin;  
  output    S, Cout;  
  
  assign {Cout, S} = A + B + Cin;  
endmodule
```

inputs/output

The diagram illustrates the components of a Verilog module declaration. The 'module name' is 'full_addr'. The 'ports' are the variables in the parameter list: 'A', 'B', 'Cin', 'S', and 'Cout'. The 'inputs/output' are the variables declared as 'input' or 'output' within the module body, and the variables used in the 'assign' statement.

Verilog Continuous Assignment

- Assignment is continuously evaluated
- `assign` corresponds to a connection or a simple component with the described function
- Target is *NEVER* a reg variable

assign A = X | (Y & ~Z);

use of Boolean operators
(~ for bit-wise, ! for logical negation)

assign B[3:0] = 4'b01XX;

bits can take on four values
(0, 1, X, Z)

assign C[15:0] = 16'h00ff;

variables can be n-bits wide
(MSB:LSB)

assign #3 {Cout, S[3:0]} = A[3:0] + B[3:0] + Cin;

use of arithmetic operator

multiple assignment (concatenation)

delay of performing computation, only used by simulator, not synthesis



Comparator Example

```
module Compare1 (A, B, Equal, Alarger, Blarger);  
    input      A, B;  
    output     Equal, Alarger, Blarger;  
  
    assign Equal = (A & B) | (~A & ~B);  
    assign Alarger = (A & ~B);  
    assign Blarger = (~A & B);  
endmodule
```

Comparator Example

```
// Make a 4-bit comparator from 4 x 1-bit comparators
```

```
module Compare4(A4, B4, Equal, Alarger, Blarger);  
    input [3:0] A4, B4;  
    output Equal, Alarger, Blarger;  
    wire e0, e1, e2, e3, A10, A11, A12, A13, B10, B11, B12, B13;  
  
    Compare1 cp0(A4[0], B4[0], e0, A10, B10);  
    Compare1 cp1(A4[1], B4[1], e1, A11, B11);  
    Compare1 cp2(A4[2], B4[2], e2, A12, B12);  
    Compare1 cp3(A4[3], B4[3], e3, A13, B13);  
  
    assign Equal = (e0 & e1 & e2 & e3);  
    assign Alarger = (A13 | (A12 & e3) |  
                     (A11 & e3 & e2) |  
                     (A10 & e3 & e2 & e1));  
    assign Blarger = (~Alarger & ~Equal);  
endmodule
```

Simple Behavioral Model: the `always` block

- `always` block
 - Always waiting for a change to a trigger signal
 - Then executes the body

```
module and_gate (out, in1, in2);  
    input    in1, in2;  
    output   out;  
    reg      out;  
  
    always @(in1 or in2) begin  
        out = in1 & in2;  
    end  
endmodule
```

Not a real register!!
A Verilog register
Needed because of
assignment in always
block

Specifies when block is executed
I.e., triggered by which signals



`always` Block

- Procedure that describes the function of a circuit
 - Can contain many statements including `if`, `for`, `while`, `case`
 - Statements in the `always` block are executed *sequentially*
 - (Continuous assignments `<=` are executed in *parallel*)
 - Entire block is executed at once
 - *Final* result describes the function of the circuit for current set of inputs
 - intermediate assignments don't matter, only the final result
- `begin/end` used to group statements



“Complete” Assignments

- If an `always` block executes, and a variable is *not* assigned
 - Variable keeps its old value (think implicit state!)
 - *NOT* combinational logic \Rightarrow latch is inserted (implied memory)

This is usually *not* what you want: dangerous for the novice!
- Any variable assigned in an `always` block should be assigned for any (and every!) execution of the block



Incomplete Triggers

- Leaving out an input trigger usually results in a sequential circuit
- Example: Output of this “and” gate depends on the input history

```
module and_gate (out, in1, in2);  
    input    in1, in2;  
    output   out;  
    reg      out;  
  
    always @(in1) begin  
        out = in1 & in2;  
    end  
  
endmodule
```

Verilog `if`

- Same as C if statement

```
// Simple 4:1 mux
module mux4 (sel, A, B, C, D, Y);
input [1:0] sel;
// 2-bit control signal
input A, B, C, D;
output Y;
reg Y;
// target of assignment
always @(sel or A or B or C or D)
    if (sel == 2'b00) Y = A;
    else if (sel == 2'b01) Y = B;
    else if (sel == 2'b10) Y = C;
    else if (sel == 2'b11) Y = D;

endmodule
```

- Another way

```
// Simple 4:1 mux
module mux4 (sel, A, B, C, D, Y);
input [1:0] sel;
// 2-bit control signal
input A, B, C, D;
output Y;
reg Y;
// target of assignment
always @(sel or A or B or C or D)
    if (sel[0] == 0)
        if (sel[1] == 0) Y = A;
        else Y = B;
    else
        if (sel[1] == 0) Y = C;
        else Y = D;

endmodule
```



Verilog case

- Sequential execution of cases
 - Only first case that matches is executed (implicit break)
 - Default case can be used

```
// Simple 4-1 mux
module mux4 (sel, A, B, C, D, Y);
input [1:0] sel;    // 2-bit control signal
input A, B, C, D;
output Y;
reg Y;              // target of assignment

    always @(sel or A or B or C or D)
        case (sel)
            2'b00: Y = A;
            2'b01: Y = B;
            2'b10: Y = C;
            2'b11: Y = D;
        endcase
endmodule
```

|
Conditions tested in
top to bottom order
↓



Verilog case

- **Note:**

```
case (case_expression)
  case_item1 : case_item_statement1;
  case_item2 : case_item_statement2;
  case_item3 : case_item_statement3;
  case_item4 : case_item_statement4;
  default   : case_item_statement5;
endcase
```

- **... is the same as ...**

```
if(case_expression == case_item1)
  case_item_statement1;
else if (case_expression == case_item2)
  case_item_statement2;
else if (case_expression == case_item3)
  case_item_statement3;
else if (case_expression == case_item4)
  case_item_statement4;
else case_item_statement5;
```

Verilog case

- Without the default case, this example would create a latch for Y
- Assigning X to a variable means synthesis is free to assign any value

```
// Simple binary encoder (input is 1-hot)
module encode (A, Y);
input  [7:0] A;           // 8-bit input vector
output [2:0] Y;           // 3-bit encoded output
reg     [2:0] Y;          // target of assignment
  always @(A)
    case (A)
      8'b00000001: Y = 0;
      8'b00000010: Y = 1;
      8'b00000100: Y = 2;
      8'b00001000: Y = 3;
      8'b00010000: Y = 4;
      8'b00100000: Y = 5;
      8'b01000000: Y = 6;
      8'b10000000: Y = 7;
      default:      Y = 3'bXXX; // Don't care when input is not 1-hot
    endcase
endmodule
```

Verilog case (cont)

- Cases are executed sequentially
 - Following implements a *priority* encoder

```
// Priority encoder
module encode (A, Y);
input  [7:0] A;          // 8-bit input vector
output [2:0] Y;          // 3-bit encoded output
reg     [2:0] Y;         // target of assignment
  always @(A)
    case (1'b1)
      A[0]:    Y = 0;
      A[1]:    Y = 1;
      A[2]:    Y = 2;
      A[3]:    Y = 3;
      A[4]:    Y = 4;
      A[5]:    Y = 5;
      A[6]:    Y = 6;
      A[7]:    Y = 7;
      default: Y = 3'bXXX; // Don't care when input is all 0's
    endcase
endmodule
```

Parallel Case

- A priority encoder is more expensive than a simple encoder
 - If we know the input is 1-hot, we can tell the synthesis tools
 - “`parallel-case`” pragma says the order of cases does not matter

```
// simple encoder
```

```
module encode (A, Y);
```

```
input  [7:0] A;           // 8-bit input vector
```

```
output [2:0] Y;           // 3-bit encoded output
```

```
reg    [2:0] Y;           // target of assignment
```

```
always @(A)
```

```
    case (1'b1)           // synthesis parallel-case
```

```
        A[0]: Y = 0;
```

```
        A[1]: Y = 1;
```

```
        A[2]: Y = 2;
```

```
        A[3]: Y = 3;
```

```
        A[4]: Y = 4;
```

```
        A[5]: Y = 5;
```

```
        A[6]: Y = 6;
```

```
        A[7]: Y = 7;
```

```
        default: Y = 3'bX; // Don't care when input is all 0's
```

```
    endcase
```

```
endmodule
```


Verilog caseX

- Like case, but cases can include 'X'
 - X bits not used when evaluating the cases
 - In other words, you don't care about those bits!

```
// Priority encoder
module encode (A, valid, Y);
input  [7:0] A; // 8-bit input vector
output [2:0] Y; // 3-bit encoded output
output valid;   // Asserted when an input is
                // not all 0's
reg  [2:0] Y; // target of assignment
reg  valid;

always @(A) begin
    valid = 1;
    caseX (A)
        8'bXXXXXXXX1: Y = 0;
        8'bXXXXXXXX10: Y = 1;
        8'bXXXXXX100: Y = 2;
        8'bXXXXX1000: Y = 3;
        8'bXXX10000: Y = 4;
        8'bXX100000: Y = 5;
        8'bX1000000: Y = 6;
        8'b10000000: Y = 7;
        default: begin
            valid = 0;
            Y = 3'bX; // Don't care when input is all
0's
        end
    endcase
end
endmodule
```

Verilog for

- **for** is similar to C
- **for** statement is executed at compile time (like macro expansion)

- Result is all that matters, not how result is calculated
- Use in testbenches only!

// simple encoder

```
module encode (A, Y);  
  input  [7:0] A;      // 8-bit input vector  
  output [2:0] Y;      // 3-bit encoded output  
  reg     [2:0] Y;      // target of assignment  
  integer i;          // Temporary variables for program only  
  reg [7:0] test;  
  always @(A) begin  
    test = 8b'00000001;  
    Y = 3'bX;  
    for (i = 0; i < 8; i = i + 1) begin  
      if (A == test) Y = i;  
      test = test << 1;  
    end  
  end  
end  
endmodule
```



Verilog `while/repeat/forever`

- `while (expression) statement`
 - Execute statement while expression is true
- `repeat (expression) statement`
 - Execute statement a fixed number of times
- `forever statement`
 - Execute statement forever



full-case **and** parallel-case

- **// synthesis parallel_case**
 - Tells compiler that ordering of cases is not important
 - That is, cases do not overlap
 - e. g., state machine - can't be in multiple states
 - Gives cheaper implementation
- **// synthesis full_case**
 - Tells compiler that cases left out can be treated as don't cares
 - Avoids incomplete specification and resulting latches




Simulating Verilog



How Are Simulators Used?

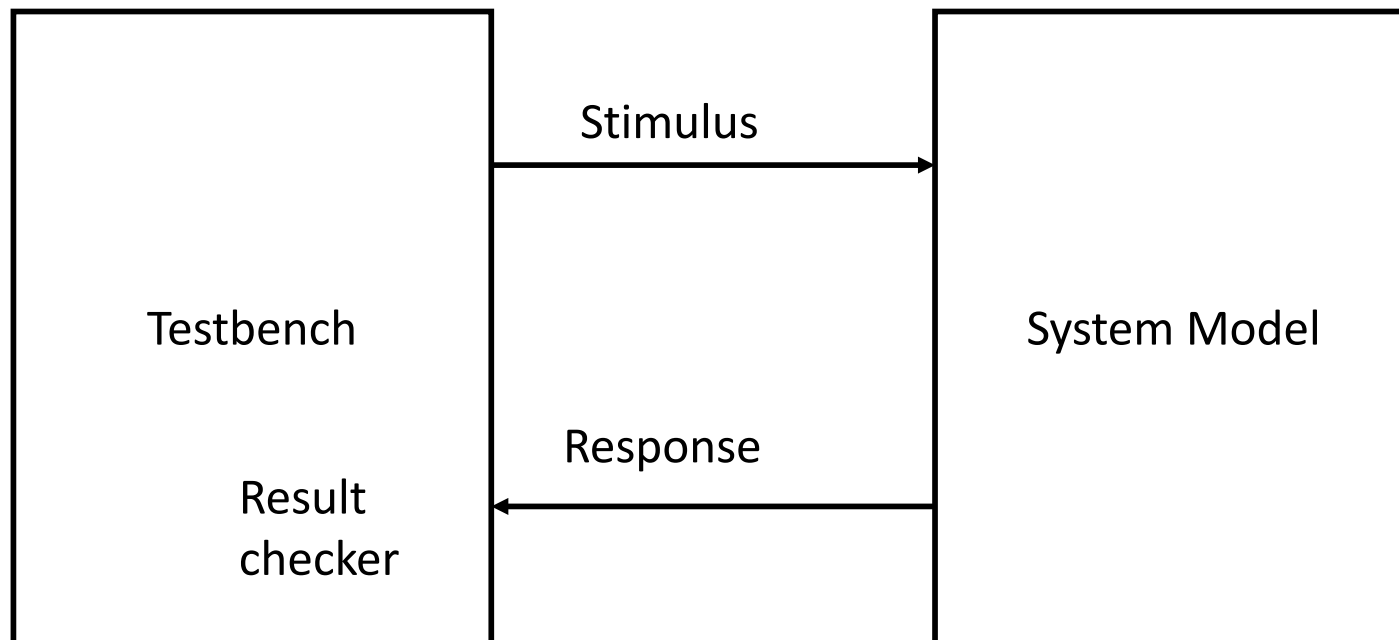- Testbench generates stimulus and checks response
- Coupled to model of the system
- Pair is run simultaneously





Writing Testbenches

```
module test;  
reg a, b, sel;
```

Inputs to device under test

```
mux m(y, a, b, sel);
```

Device under test

```
initial begin
```

\$monitor is a built-in event
driven “printf”

```
    $monitor($time,, “a = %b b=%b sel=%b y=%b”,  
              a, b, sel, y);
```

```
    a = 0; b = 0; sel = 0;
```

```
    #10 a = 1;
```

```
    #10 sel = 1;
```

```
    #10 b = 1;
```

```
end
```

Stimulus generated by
sequence of assignments
and delays



Simulation Behavior

- Scheduled using an event queue
- Non-preemptive, no priorities
- A process must explicitly request a context switch
- Events at a particular time unordered
- Scheduler runs each event at the current time, possibly scheduling more as a result



Two Types of Events

- Evaluation events compute functions of inputs
- Update events change outputs
- Split necessary for delays, nonblocking assignments, etc.

Update event writes
new value of a and
schedules any
evaluation events that
are sensitive to a
change on a

$$a \leq b + c$$

Evaluation event reads
values of b and c, adds
them, and schedules an
update event



Simulation Behavior

- Concurrent processes (initial, always) run until they stop at one of the following
 - #42
 - Schedule process to resume 42 time units from now
 - wait(cf & of)
 - Resume when expression “cf & of” becomes true
 - @(a or b or y)
 - Resume when a, b, or y changes
 - @(posedge clk)
 - Resume when clk changes from 0 to 1



Simulation Behavior

- Infinite loops are possible and the simulator does not check for them
- This runs forever: no context switch allowed, so ready can never change

```
while (~ready)  
    count = count + 1;
```

- Instead, use

```
wait(ready);
```



Simulation Behavior

- Race conditions abound in Verilog
- These can execute in either order: final value of a undefined:

```
always @(posedge clk) a = 0;  
always @(posedge clk) a = 1;
```



Simulation Behavior

- Semantics of the language closely tied to simulator implementation
- Context switching behavior convenient for simulation, not always best way to model
- Undefined execution order convenient for implementing event queue

Testbenches (ModelSim)

Full Adder (1-bit)

```
module full_adder (a, b, cin,
                  sum, cout);
    input  a, b, cin;
    output sum, cout;
    reg    sum, cout;

    always @(a or b or cin)
    begin
        sum = a ^ b ^ cin;
        cout = (a & b) | (a & cin) | (b & cin);
    end
endmodule
```

Full Adder (4-bit)

```
module full_adder_4bit (a, b, cin, sum,
                       cout);
    input[3:0] a, b;
    input      cin;
    output [3:0] sum;
    output      cout;
    wire       c1, c2, c3;

    // instantiate 1-bit adders
    full_adder FA0(a[0],b[0], cin, sum[0], c1);
    full_adder FA1(a[1],b[1], c1, sum[1], c2);
    full_adder FA2(a[2],b[2], c2, sum[2], c3);
    full_adder FA3(a[3],b[3], c3, sum[3], cout);
endmodule
```


Testbench

```
module test_adder;
    reg [3:0] a, b;
    reg      cin;
    wire [3:0] sum;
    wire      cout;

    full_adder_4bit dut(a, b, cin,
                       sum, cout);


    initial
    begin
        a = 4'b0000;
        b = 4'b0000;
        cin = 1'b0;
        #50;
        a = 4'b0101;
        b = 4'b1010;
        // sum = 1111, cout = 0
        #50;
        a = 4'b1111;
        b = 4'b0001;
        // sum = 0000, cout = 1
        #50;
        a = 4'b0000;
        b = 4'b1111;
        cin = 1'b1;
        // sum = 0000, cout = 1
        #50;
        a = 4'b0110;
        b = 4'b0001;
        // sum = 1000, cout = 0
        end // initial begin
    endmodule // test_adder
```

ModelSim Simulation

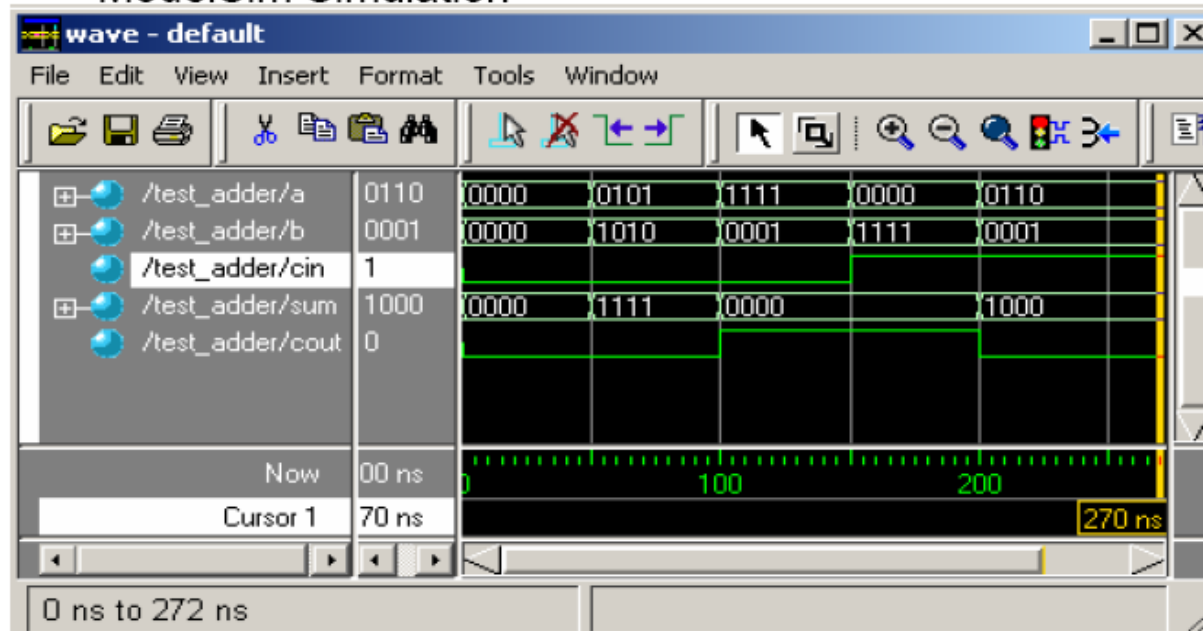

Vivado

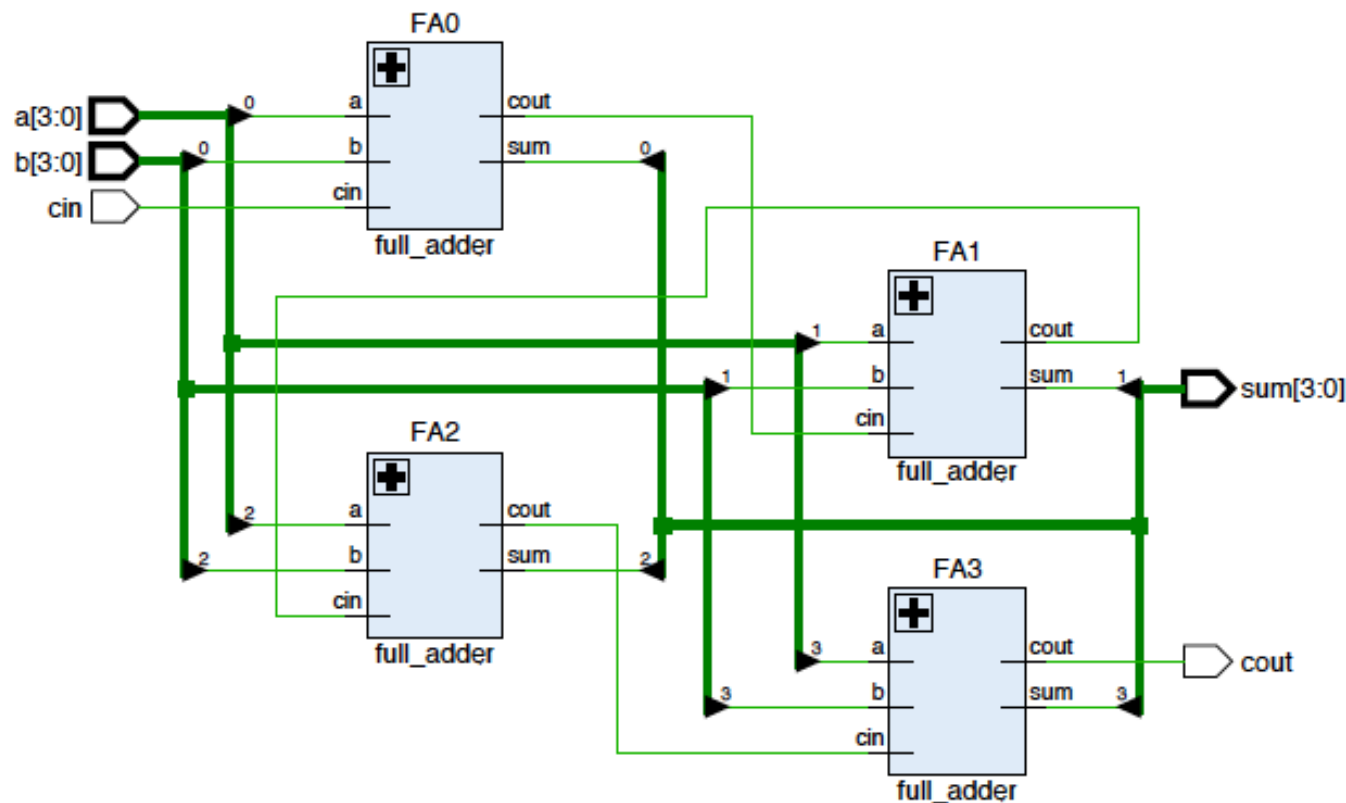- The exact same code from modelsim was used in Vivado 2016.2
- The elaboration of the code produced the following schematic



Testbench Vivado

The screenshot displays the Vivado IDE interface for a behavioral simulation of a 4-bit adder testbench. The main window shows the simulation results for the testbench, with a table of signal values and a waveform view.

Scopes

Name	Design Unit	Block Type
test_adder	test_adder	Verilog Module
dut	full_adder_4bit	Verilog Module
gbl	gbl	Verilog Module

Objects

Name	Value	Data Type
a[3:0]	0110	Array
b[3:0]	0001	Array
cin	1	Logic
sum[3:0]	1000	Array
cout	0	Logic

Simulation Scope Properties

Name: /test_adder
Design unit: test_adder
Block type: Verilog Module
File: [Z:/Documents/fulladdertestverilog/test_adder.v](#)

Tcl Console

```
# run 250ns
xsim: Time (s): cpu = 00:00:02 ; elapsed = 00:00:38 . Memory (MB): peak = 1088.789 ; gain = 6.777
INFO: [USF-XSim-96] XSim completed. Design snapshot 'test_adder_behav' loaded.
INFO: [USF-XSim-97] XSim simulation ran for 250ns
launch_simulation: Time (s): cpu = 00:00:03 ; elapsed = 00:01:39 . Memory (MB): peak = 1088.789 ; gain = 6.777
```